

$$V_{avg} = \frac{1}{\pi} \int_0^{\pi} V_0 d\omega t = \frac{1}{\pi} \int_0^{\pi} V_m \sin(\omega t) d\omega t$$

$$= \frac{1}{\pi} V_m \left[-\cos \omega t \right]_0^{\pi}$$

$$= \frac{V_m}{\pi} [-1 - (-1)] = \boxed{\frac{2V_m}{\pi} = V_{avg.}}$$

$$V_{rms} = \left[\frac{1}{\pi} \int_0^{\pi} V_0^2 d\omega t \right]^{1/2}$$

$$= \left[\frac{1}{\pi} \int_0^{\pi} (V_m)^2 \sin^2 \omega t d\omega t \right]^{1/2}$$

$$= \left[\frac{(V_m)^2}{\pi} \int_0^{\pi} \left(\frac{1 - \cos 2\omega t}{2} \right) d\omega t \right]^{1/2}$$

$$= \left[\left(\frac{(V_m)^2}{2\pi} \right) \left[\omega t \right]_0^{\pi} - \left[\frac{\sin 2\omega t}{2} \right]_0^{\pi} \right]^{1/2}$$

$$= \left(\frac{(V_m)^2 \cdot \pi}{2\pi} \right)^{1/2} = \frac{V_m}{\sqrt{2}}$$

$$\boxed{V_{rms} = \frac{V_m}{\sqrt{2}}}$$

Form factor

$$F.F. = \frac{V_{rms}}{V_{avg}} = \frac{V_m \pi}{\sqrt{2} (2V_m)} = \frac{\pi}{2\sqrt{2}} = 1.11$$

Ripple factor

$$r = \sqrt{(F.F.)^2 - 1} = \sqrt{1.2321 - 1} = \sqrt{0.2321}$$

$$r = 0.48$$

$$\boxed{r\% = 48}$$

$$\text{Efficiency } (\%) = \frac{\text{output power (dc)}}{\text{input power (ac)}} \times 100$$

$\rightarrow I_{rms}$

For Full-wave

$$= \frac{(I_{dc})^2 R_L \times 100}{(I_{rms})^2 R_L} = \frac{(I_{dc})^2 \times 100}{(I_{rms})^2} = \left(\frac{V_{dc}}{V_{rms}} \right)^2 \times 100$$


$$= \left(\frac{2V_m}{\pi} \right)^2 \left(\frac{\sqrt{2}}{V_m} \right)^2 \times 100 = \frac{4 \times 2}{\pi^2} \times 100 = 81.13$$

for Half-wave:

$$\eta = \left(\frac{I_m}{\pi} \right)^2 \left(\frac{2}{I_m} \right)^2 \times 100 = \frac{4 \times 100}{\pi^2} = 40.56$$

Ques

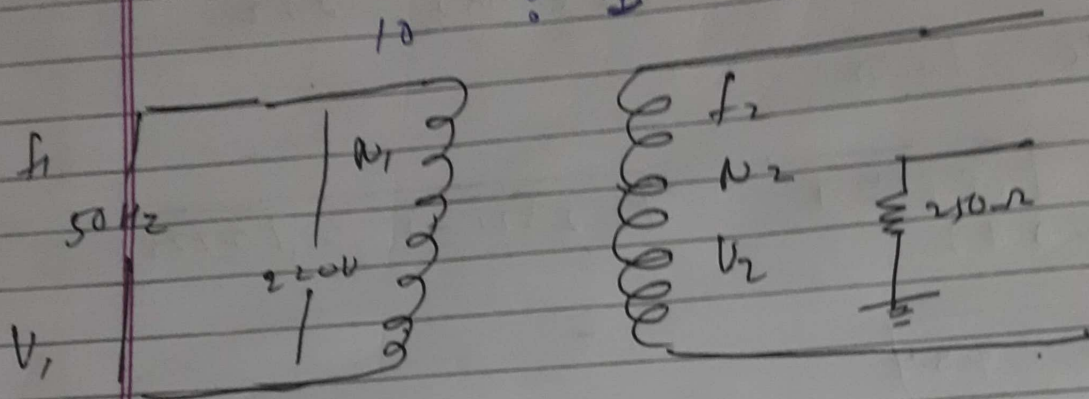For the given circuit find out the dc output voltage, rectification efficiency, peak inverse voltage, output frequency



$$\frac{N_1}{N_2} = \frac{10}{1} = \frac{V_1}{V_2} \Rightarrow V_2 = \frac{V_1}{10} = \frac{220}{10} = 22 \text{ V}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \Rightarrow V_m = 22\sqrt{2} \text{ V}$$

$$V_c = V_m \sin(2\pi f t)$$

$$V_c = 22\sqrt{2} \sin(50t)$$

$$V_{dc} = \frac{2V_m}{\pi} = \frac{2 \times 22\sqrt{2}}{\pi} = \frac{44\sqrt{2}}{\pi} \text{ V}$$

$$\eta = 48\%$$

$$\eta = \frac{44\sqrt{2}}{\pi \times 22} \times 100$$

$$\eta = 48\%$$

$$T_r = 2T_1$$




$$\frac{1}{f_1} = \frac{2}{f_2} \Rightarrow f_2 = 2f_1 = 100 \text{ Hz}$$

For peak inverse voltage.

$V_m = V_{\text{inverse}} = V_m \Rightarrow$ for bridge.

$V_{\text{inverse}} = 2V_m \Rightarrow$ centre Tap

Avalanche & Zener Diode.

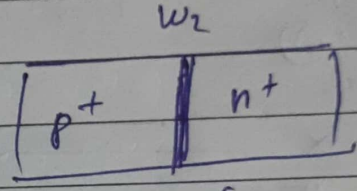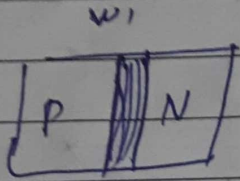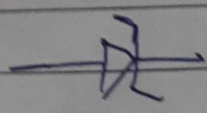

For
forward



I_{f1}

$w_1 > w_2$
 $I_{f2} > I_{f1}$

I_{f2}


for
Reverse

$w_2 > w_1$

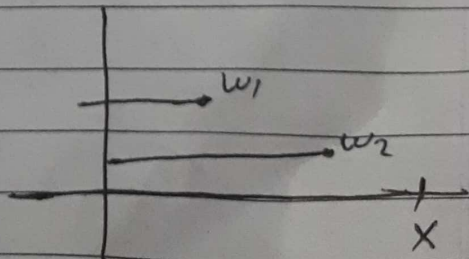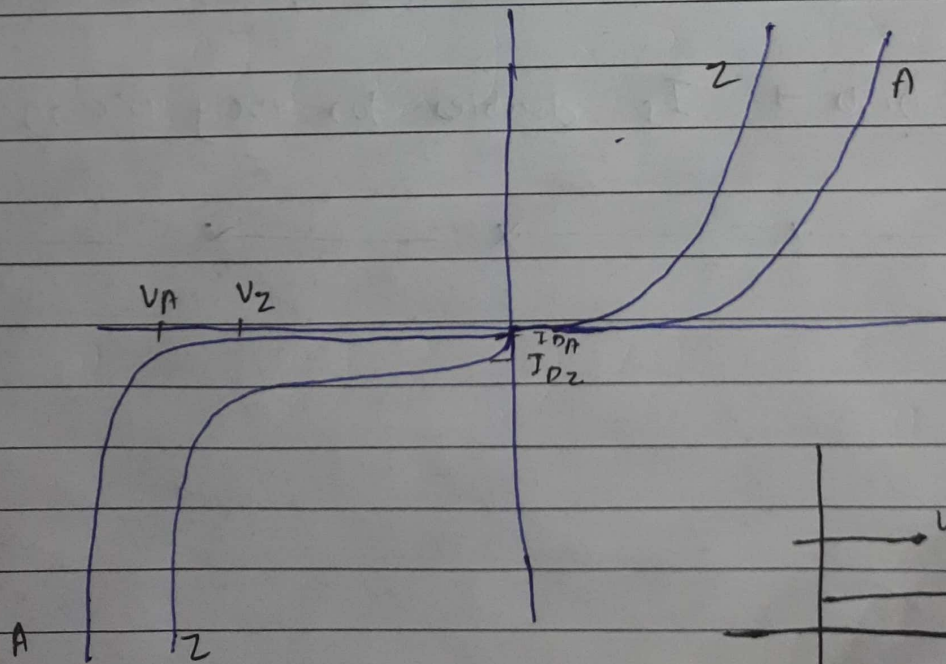

Zener reaches break down
first.

Effects of temp. on V-I characteristics

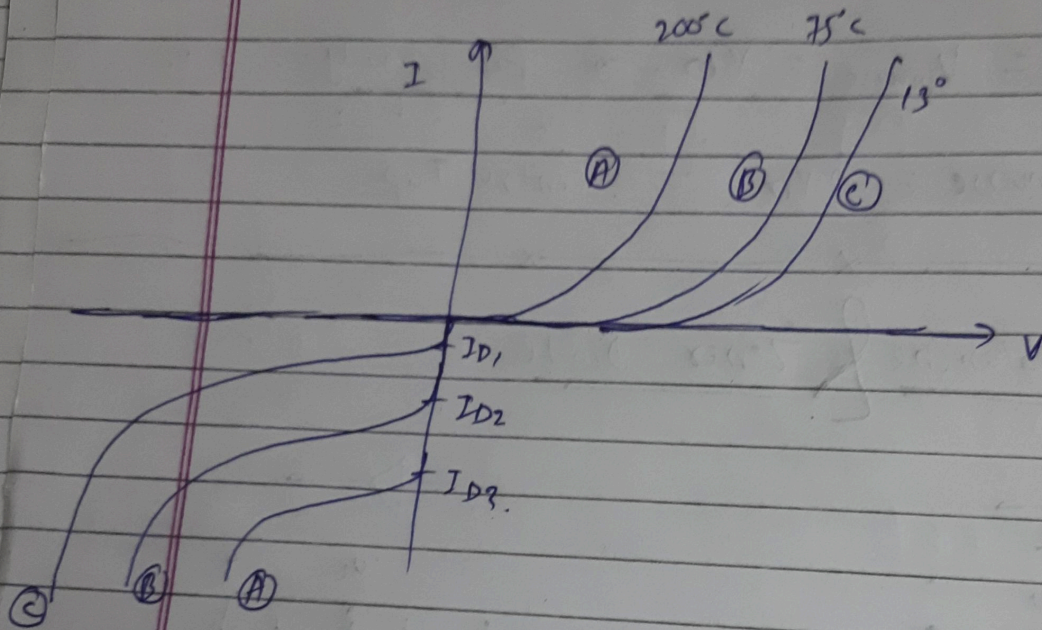

#

Effect of Temperature on V-I characteristics

- a) forward bias → for Si diode, it shifts to left at rate of 2.5mV per degree rise in temp.
- b) Reverse bias → I_s doubles for every 10°C rise in temp.